

RADHIKA PATWARI

18CS10062

PAGE NO.

DATE 21/10/2020

COA LAB TEST 1

1. (a)

$$Z = XYS_3 + X\bar{Y}S_2 + \bar{X}YS_1 + \bar{X}\bar{Y}S_0$$

(b) (a) For $S = 0110$
 $S_3 S_2 S_1 S_0$

$$\therefore S_3 = 0, S_2 = 1, S_1 = 1, S_0 = 0$$

$$\therefore Z = XY(0) + X\bar{Y}(1) + \bar{X}Y(1) + \bar{X}\bar{Y}(0)$$

$$\Rightarrow Z = 0 + X\bar{Y} + \bar{X}Y + 0$$

$$\Rightarrow \boxed{Z = X\bar{Y} + \bar{X}Y}$$

(b) For $S = 0011$
 $S_3 S_2 S_1 S_0$

$$S_3 = 0, S_2 = 0, S_1 = 1, S_0 = 1$$

$$\therefore Z = XY(0) + X\bar{Y}(0) + \bar{X}Y(1) + \bar{X}\bar{Y}(1)$$

$$\Rightarrow Z = 0 + 0 + \bar{X}Y + \bar{X}\bar{Y}$$

$$\Rightarrow \boxed{Z = \bar{X}Y + \bar{X}\bar{Y}}$$

(c) (a) For XOR function,

$$\begin{aligned} Z &= X\bar{Y} + \bar{X}Y \\ &= XY(0) + X\bar{Y}(1) + \bar{X}Y(1) + \bar{X}\bar{Y}(0) \end{aligned}$$

$$\therefore S_3=0, S_2=1, S_1=1, S_0=0$$

$$\therefore \boxed{S = 0110}$$

(b) OR function,

$$\begin{aligned} Z &= X+Y \\ &= X(Y+\bar{Y}) + Y(X+\bar{X}) \\ &= XY + X\bar{Y} + X\bar{Y} + \bar{X}Y \\ &= XY + X\bar{Y} + \bar{X}Y \\ &= \underset{S_3}{XY(1)} + \underset{S_2}{X\bar{Y}(1)} + \underset{S_1}{\bar{X}Y(1)} + \underset{S_0}{\bar{X}\bar{Y}(0)} \end{aligned}$$

$$A+\bar{A}=1$$

$$\therefore \boxed{S = 1110}$$

$$\begin{aligned} \underline{2.} \quad Aol(a, b, c, d) &= ((a \wedge b) \vee (c \wedge d)) \\ &= ((ab) + (cd)) \end{aligned}$$

$$1 \neq e(v, g, h) = vg + v'h$$

$$\begin{aligned}
 A01 &= (ab + cd)' = (ab)' \cdot (cd)' \\
 &= (a' + b')(c' + d') \\
 &= \underline{a'c'} + \underline{a'd'} + \underline{b'c'} + \underline{b'd'} \\
 &\quad + a \cdot 0 + b \cdot 0
 \end{aligned}$$

$$ITE(a, 0, 1) = a \cdot 0 + a' \cdot 1 = a'$$

$$ITE(b, 0, 1) = b \cdot 0 + b' \cdot 1 = b'$$

$$ITE(c, 0, 1) = c \cdot 0 + c' \cdot 1 = c'$$

$$ITE(d, 0, 1) = d \cdot 0 + d' \cdot 1 = d'$$

$$ITE(\cancel{a}, 0, ITE(c, 0, 1))$$

$$= a \cdot 0 + a'c'$$

$$ITE(b, 0, ITE(c, 0, 1))$$

$$= b \cdot 0 + b'c'$$

$$ITE(a, 0, ITE(d, 0, 1))$$


$$= a \cdot 0 + a'd'$$

$$ITE(b, 0, ITE(d, 0, 1))$$

$$= b \cdot 0 + b'd'$$

$$\begin{aligned}
 \therefore AOI &= ITE(a, 0, ITE(c, 0, 1)) \\
 &+ ITE(b, 0, ITE(c, 0, 1)) \\
 &+ ITE(a, 0, ITE(d, 0, 1)) \\
 &+ ITE(b, 0, ITE(d, 0, 1))
 \end{aligned}$$
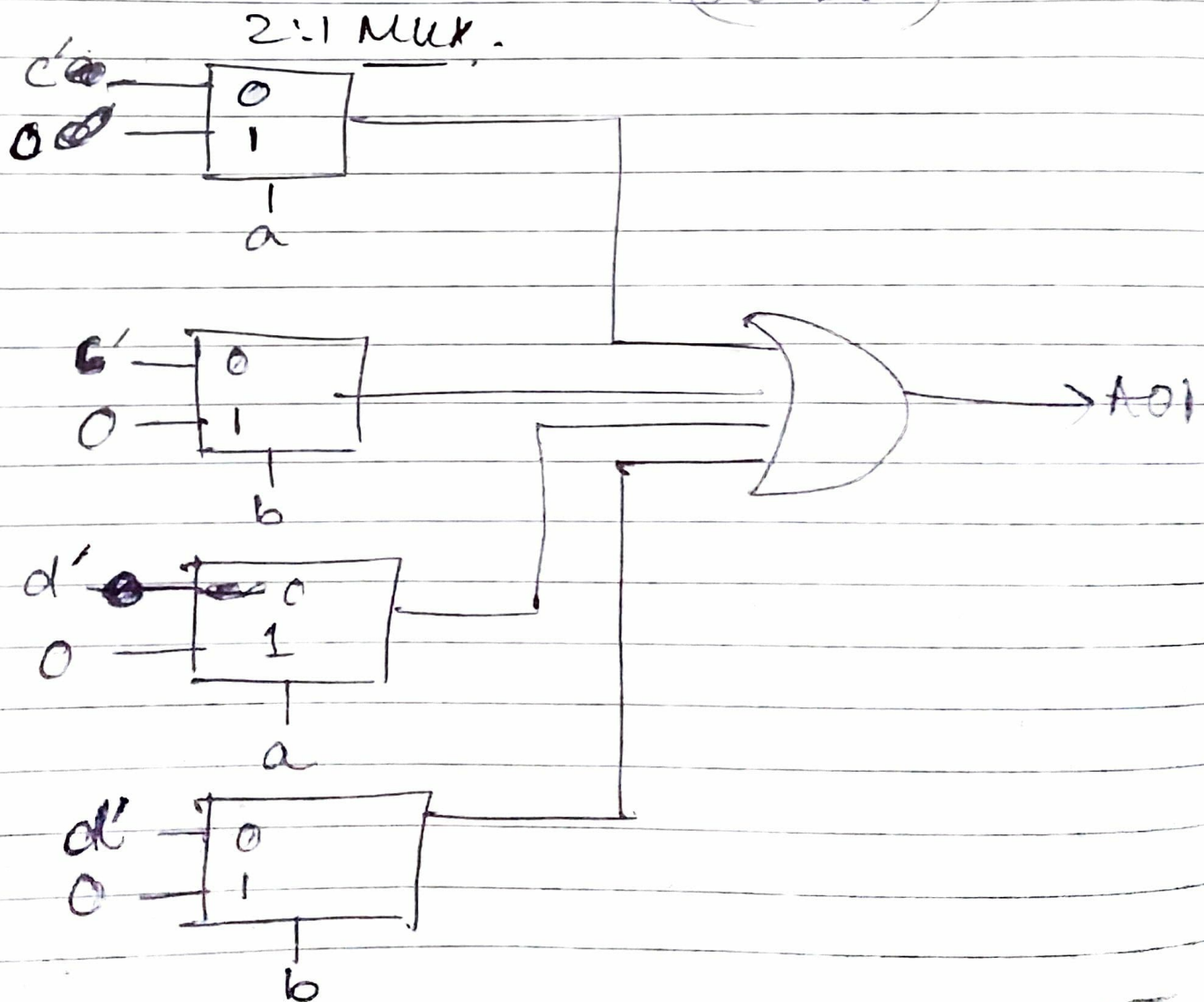
$$AOI = (a \cdot 0 + a'c') + (b \cdot 0 + b'c') + (a \cdot 0 + a'd') + (b \cdot 0 + b'd')$$



3. $X = n$ bit unsigned binary no.

Let 2's complement of $X = P$.

Let $X = 0X_{n-2}X_{n-3} \dots X_1X_0$

$$\therefore P = (\overline{0} \cdot \overline{X_{n-2}} \cdot \overline{X_{n-3}} \dots \overline{X_1} \cdot \overline{X_0}) + \underbrace{00 \dots 1}_{n-1 \text{ times}}$$

~~$$= (1 \oplus 0) \cdot (1 \oplus X_{n-2}) \cdot (1 \oplus X_{n-3}) \dots (1 \oplus X_1) \cdot (1 \oplus X_0)$$~~

~~$$= 1000 \dots 1$$~~

$$= \underbrace{1111 \dots 1}_{n \text{ bits}} \oplus 0X_{n-2}X_{n-3} \dots X_1X_0 + \underbrace{00 \dots 1}_{n-1 \text{ times}}$$


$$= (\underbrace{1000 \dots 1}_{n \text{ bits}} - \underbrace{000 \dots 1}_{n-1 \text{ times}}) \oplus 0X_{n-2}X_{n-3} \dots X_1X_0$$

$$= (2^n - 1) \oplus X + \underbrace{00 \dots 1}_{n-1 \text{ times}}$$

$$= 2^n \oplus X$$


$$\therefore P = 2 \text{'s complement of } X = \underline{\underline{2^n - X}}$$

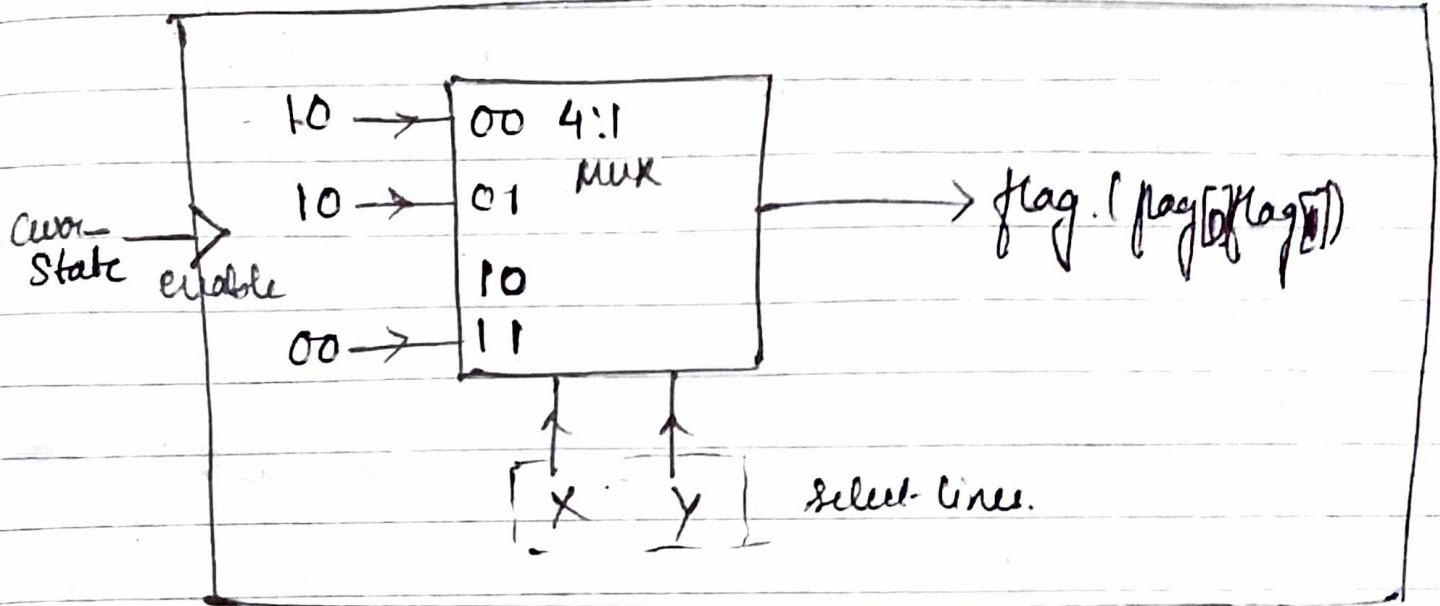5. Let $\text{curr-state}[0] = x$
 $\text{curr-state}[1] = y$



For the mux, $\text{flag}[0] = (\text{curr-state}[0])'(\text{curr-state}[1])' + (\text{curr-state}[0])(\text{curr-state}[1])$


$$\text{flag}[1] = 0$$

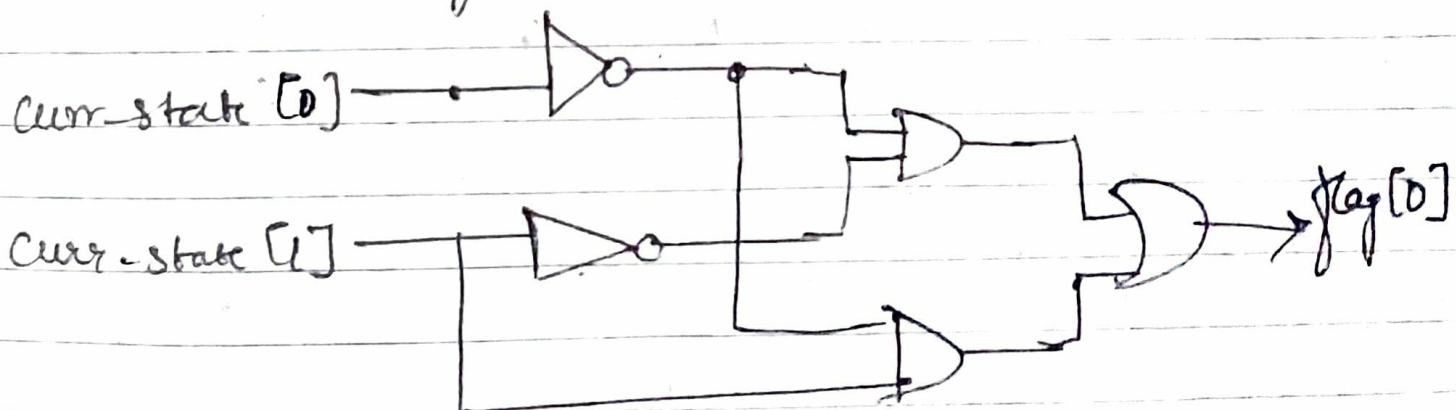

0 $\xrightarrow{\text{flag}[1]}$


6. Half adder $S = A \oplus B = A \oplus B$
 $C = A \cdot B = ((AB)')'$
 $= (A' + B')'$

Half adder circuit,

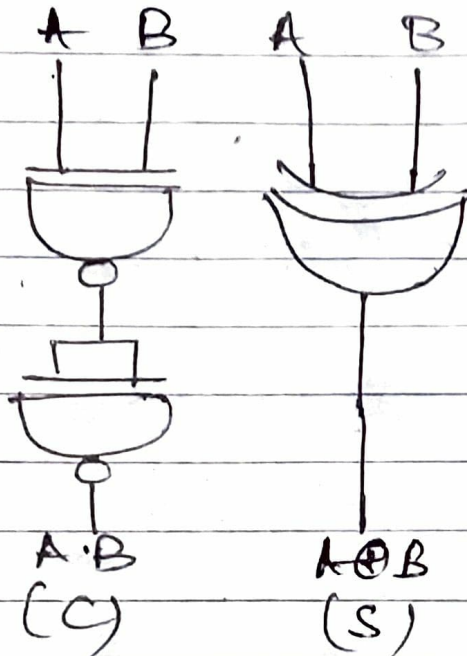


For OR gate
 $= ((A+B)')'$
 $= (A'B')'$

Full adder circuit

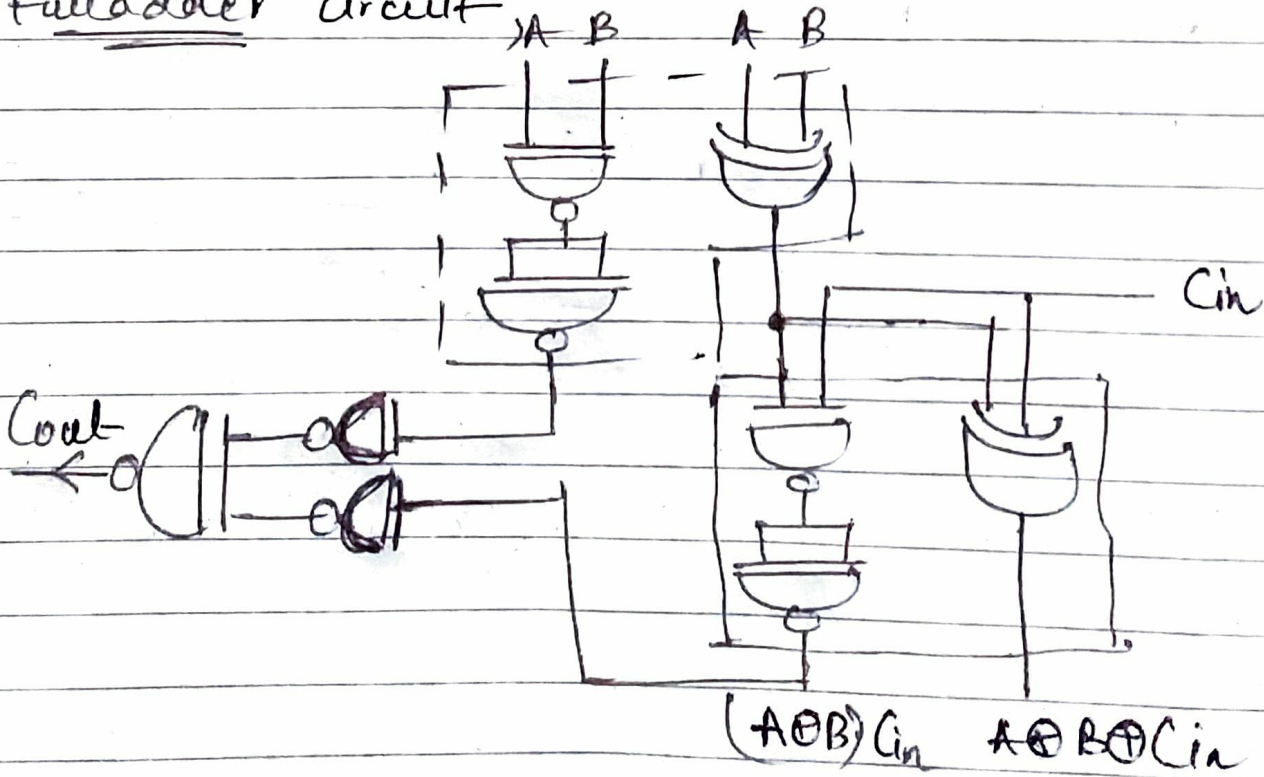

Optimised full adder,

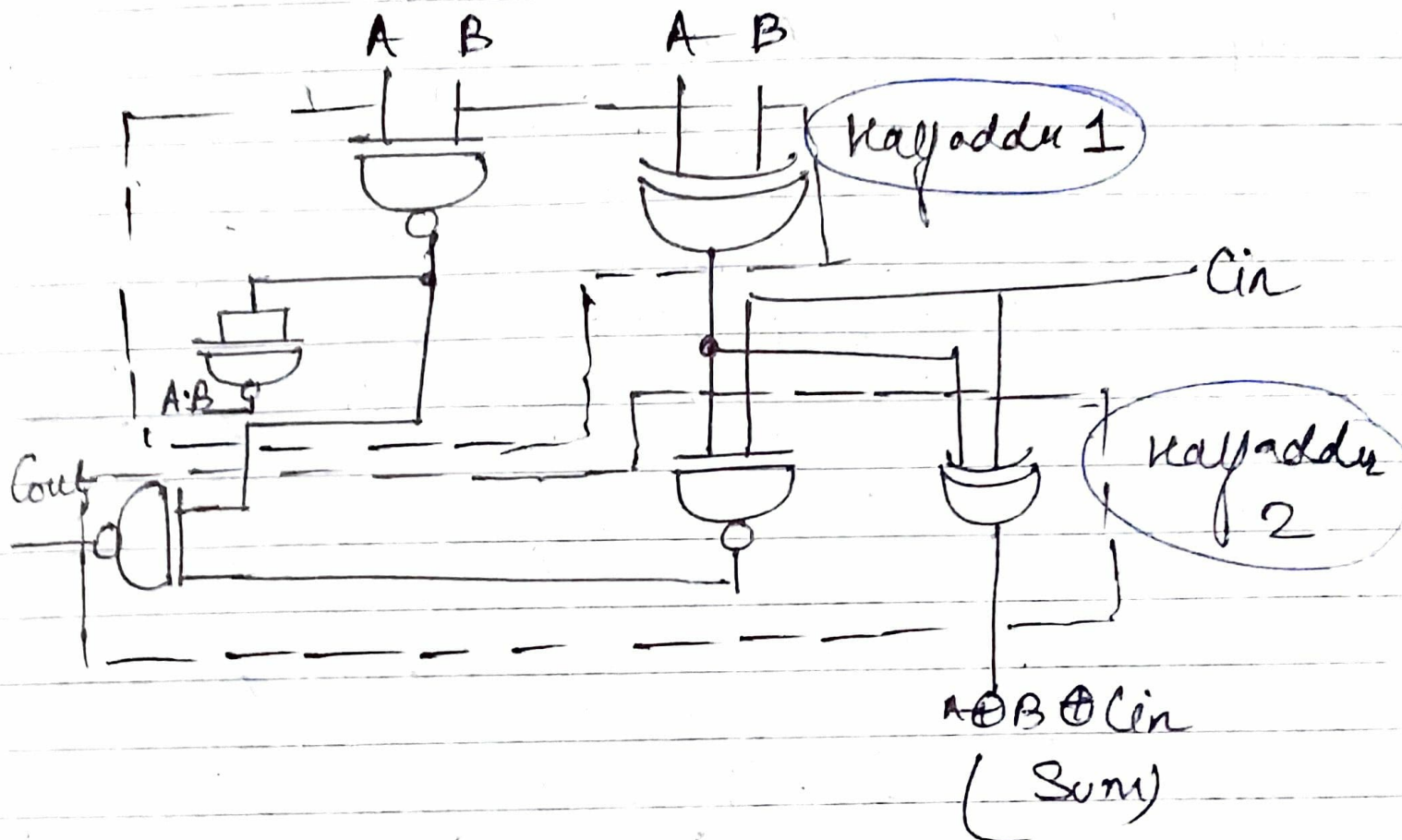

Using 2 Half Adders in full adder,

1 full adder has worst case delay

$$\Rightarrow t_{KOR} + 3t_{NAND}$$

$\therefore n \text{ bit RCA} = n \text{ full adders}$

$$\underline{\text{Total delay} = n(t_{KOR} + 3t_{NAND})}$$

7. (a)

$$C_{i+1} = g_i + \sum_{j=0}^{i-1} \kappa_{jk} g_j p_k + \left(\sum_{k=0}^i \kappa p_k \right) c_0$$

$$C_{i+1} = g_i + p_i c_i$$

(b)

$$C_{i+1}' = (g_i + p_i c_i)'$$

$$= (x_i y_i + (x_i \oplus y_i) c_i)'$$

$$= (x_i y_i)' \cdot [(x_i \oplus y_i)' + c_i']$$


$$= (x_i y_i)' [(x_i y_i' + x_i' y_i)' + c_i']$$

~~$$=$$~~

7. (c) $c_{i+1} = g_i + \sum_{j=0}^{i-1} \prod_{k=j+1}^i g_j p_k + \left(\prod_{k=0}^i p_k \right) c_0$

(d) (a) One OR gate with 3 inputs.

(b) i AND gates

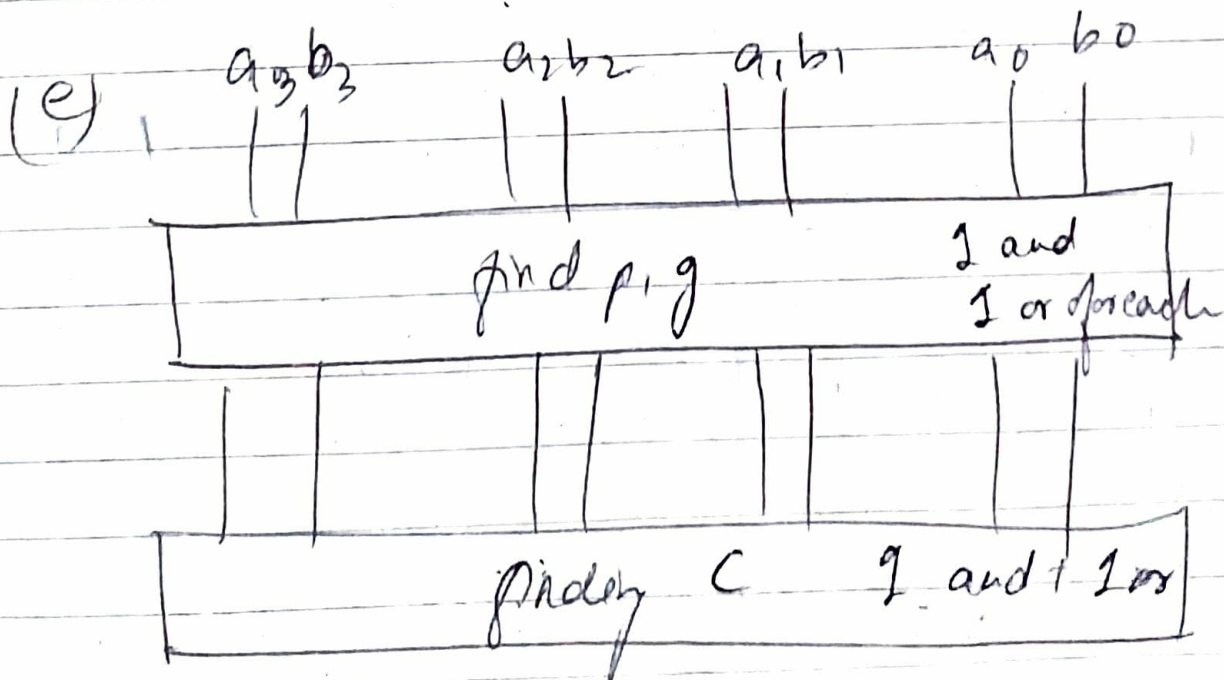

for carry $\rightarrow 4 \text{ ~~and~~ } (2 t_{AND,2} + 2 t_{OR,2})$

~~for carry~~

$$\begin{aligned}
 7.(b) \quad \overline{C_{i+1}} &= \text{~~and~~} (x_i c_i + x_i y_i + y_i c_i)' \\
 &= (x_i c_i)' \cdot (x_i y_i)' (y_i c_i)' \\
 &= (x_i' + c_i') (x_i' + y_i') (y_i' + c_i') \\
 &= (x_i' + x_i' y_i' + c_i' x_i' + c_i' y_i') (y_i' + c_i') \\
 &= x_i' y_i' + x_i' c_i' + \cancel{x_i' y_i' + x_i' y_i' c_i'} \\
 &\quad + c_i' x_i' y_i' + \cancel{c_i' x_i' + c_i' y_i'} \\
 &= \underbrace{x_i' y_i' + x_i' c_i' + x_i' y_i' c_i' + y_i' c_i'} \\
 &= (x_i + y_i)' + x_i' c_i' (1 + y_i') + y_i' c_i' \\
 &= (x_i + y_i)' + x_i' c_i' + y_i' c_i' \\
 &= k_i^0 + (x_i' + y_i') x_i' c_i' \\
 &= k_i^0 + \underbrace{(x_i' y_i + x_i' y_i')}_{k_i} + \underbrace{(y_i' x + y_i' x_i')}_{k_i} c_i' \\
 &= k_i^0 + (k_i^0 + p_i^0) c_i'
 \end{aligned}$$

$$\therefore \boxed{\bar{C}_{i+1} = k_i + (k_i + p_i) \bar{C}_i}$$

4. Yes Booth's algo has advantage as

In ordinary add-subtract, Y is multiplied by each bit of X in sequence & the results are summed up so that X^2 's contribution to the product $P = XY$ is

$$\sum_{j=i-k}^{i-1} 2^j Y$$

Now in Booth's algo, it performs addition only on seeing $x_{i-k}x_{i-k-1} = 01$ which contributes to $2^j Y$ to P . It performs a subtraction at

$x_{i-k}x_{i-k-1} = 10$ which contributes to $-2^{i-k} Y$ to P . Thus net contribution is

$$\begin{aligned} 2^i Y - 2^{i-k} Y &= 2^{i-k} Y (2^k - 1) \\ &= 2^{i-k} \sum_{m=0}^{k-1} 2^m Y \end{aligned}$$

$$= \sum_{m=0}^{k-1} 2^{m+k} y$$